

电子线路设计、测试与实验

实验报告（七）

实验名称：EDA 多功能数字钟

学院： 电子信息与通信学院

专业班级： 提高 2201 班

姓名： 王翎羽

学号： U202213806

目录

一、	实验名称	1
二、	实验目的	1
三、	实验任务	1
1.	功能要求	1
2.	验收内容	1
四、	实验原理	1
1.	状态图的描述方法	1
2.	脉冲分配器设计步骤	1
3.	自顶而下的设计方法	2
五、	实验过程	2
1.	步进电机代码	2
2.	步进电机仿真输出结果	4
3.	数字钟代码	6
4.	数字钟的插板结果	错误!未定义书签。
六、	实验小结	19

第七次实验：有限状态机及数字钟

一、实验名称

有限状态机及数字钟

二、实验目的

1. 掌握用 verilog HDL 描述数字逻辑电路与系统的方法；
2. 有限状态机概念；
3. 掌握用 verilog HDL 描述有限状态机的方法；
4. 掌握分层次电路设计方法；
5. 熟练掌握数字钟的设计与调试方法。

三、实验任务

步进电机脉冲分配器设计与多功能数字钟设计

1. 功能要求

1. 使用组合逻辑，能显示小时、分钟、秒钟
2. 能调整小时、分钟的时间。

2. 验收内容

代码及实验板实操结果

四、实验原理

1. 状态图的描述方法


1. 利用 parameter 描述状态机中各个状态的名称，并指定状态编码。例如，对序列检测器的状态分配使用最简单的自然二进制码，其描述如下：`parameter S0=2'b00, S1=2'b01, S2=2'b10, S3 = 2'b11;`
2. 用 always 块描述状态触发器实现状态存储。
3. 使用敏感表和 case 语句 (也可以采用 if-else 等价语句) 描述的状态转换逻辑。
4. 描述状态机的输出逻辑。

2. 脉冲分配器设计步骤

1. 创建子目录 E:\EDA_Lab\Lab5，并新建一个工程项目。
2. 使用 Verilog HDL 设计电路，并进行仿真分析。
3. 用 FPGA 开发板实现步进电机脉冲分配器，并实际测试逻辑功能。(A、B、C 用发光二极管代替)。
4. 根据实验流程和实验结果，写出实验总结报告，并对波形图和实验现象进行说明。

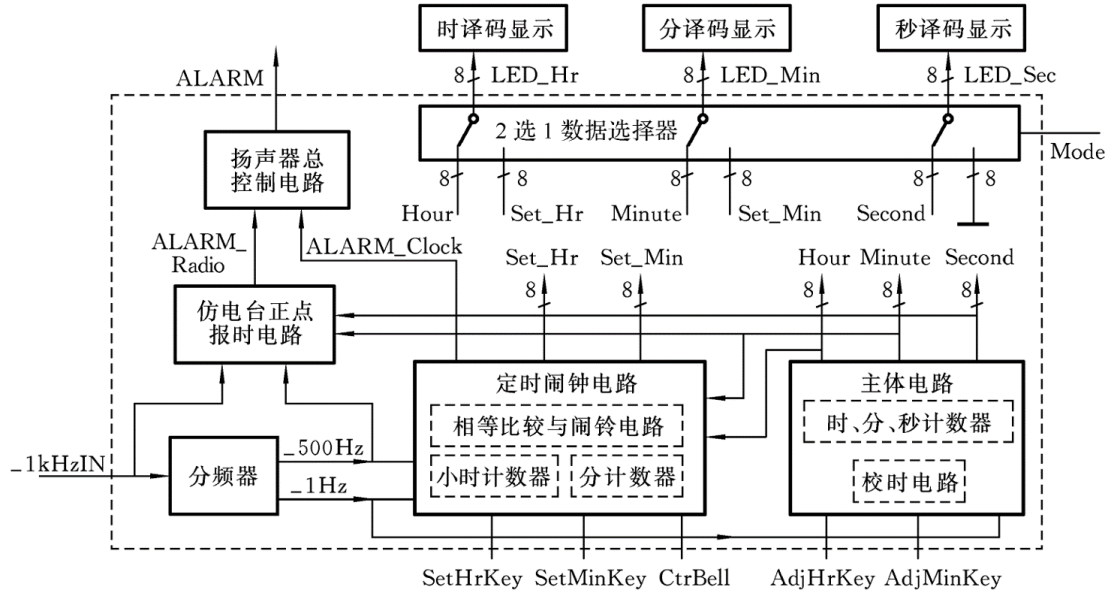3. 自顶而下的设计方法

先设计顶层总框图,该框图由若干个具有特定功能的源模块组成。下一步针对这些具有不同功能的模块进行设计,对于有些功能复杂的模块,还可以将该模块继续化分为若干个功能子模块,这样就形成模块套模块的层次化设计方法。



五、实验过程

1. 有限状态机设计代码

1. 分频器模块

```
module clk_divider (
    input clk_125MHz,
    input rst_n,
    output reg clk_1Hz
);
```

reg [26:0] count; // 27 位计数器, 用于计数 125M 时钟的周期数

```
always @(posedge clk_125MHz or negedge rst_n) begin
    if (!rst_n) begin
        count <= 0;
        clk_1Hz <= 0;
    end else begin
        if (count == 100_000_000) begin
            count <= 0;
            clk_1Hz <= ~clk_1Hz; // 1 秒翻转一次
        end
    end
end
```

```

        end else begin
            count <= count + 1;
        end
    end
end
endmodule

```

2. 步进模块

```

module fsm (
    input clk, // 时钟信号
    input rst_n, // 复位信号 (低电平有效)
    input A, // 输入信号 A
    output reg [2:0] state // 输出当前状态
);

parameter S0 = 3'b000,
           S1 = 3'b001,
           S2 = 3'b010,
           S3 = 3'b011,
           S4 = 3'b100,
           S5 = 3'b101,
           S6 = 3'b110,
           S7 = 3'b111;

reg [2:0] next_state; // 下一个状态

// 状态机逻辑
always @(posedge clk or negedge rst_n) begin
    if (!rst_n) begin
        state <= S0; // 复位时状态置为 S0
    end else begin
        state <= next_state; // 正常情况下根据
next_state 更新状态
    end
end

// 组合逻辑, 根据当前状态和输入信号 A 更新下一个状态
always @(*) begin
    case(state)
        S0: next_state = A ? S6 : S6;
        S1: next_state = A ? S3 : S5;
        S2: next_state = A ? S6 : S3;
        S3: next_state = A ? S2 : S1;
    endcase
end

```

```

        S4: next_state = A ? S5 : S6;
        S5: next_state = A ? S1 : S4;
        S6: next_state = A ? S4 : S2;
        S7: next_state = A ? S0 : S0;
        default: next_state = S0;
    endcase
end

endmodule

3. 顶层模块
module top (
    input clk_125MHz,
    input rst_n,
    input A,
    output wire [2:0] state
);

    wire clk_1Hz;

    clk_divider divider (
        .clk_125MHz(clk_125MHz),
        .rst_n(rst_n),
        .clk_1Hz(clk_1Hz)
    );

    fsm fsm_inst (
        .clk(clk_1Hz),
        .rst_n(rst_n),
        .A(A),
        .state(state)
    );

endmodule

```

1. 有限状态机测试代码和仿真结果

1. 仿真代码

```

`timescale 1ns / 1ps

module fsm_tb;

    reg clk;
    reg rst_n;

```

```
reg A;
wire [2:0] state;

fsm dut (
    .clk(clk),
    .rst_n(rst_n),
    .A(A),
    .state(state)
);

// 时钟信号生成
always #5 clk = ~clk;

// 初始化
initial begin
    clk = 0;
    rst_n = 0;
    A = 0;
    #10;
    rst_n = 1;
    #10;


    // 循环激励状态机
    repeat (5) begin
        A = 1;
        #10;
        A = 0;
        #10;
    end

    $finish;
end

// 打印状态
always @(state) begin
    $display("State: %b", state);
end

endmodule
```

2. 仿真结果

 

3. 数字钟代码

1. 顶层文件

```

`timescale 1ns / 1ps

module Clock(
    input wire clock_en,
    input wire CR,
    input wire CP,
    input wire adjust_hour_en,
    input wire adjust_minute_en,
    input wire second_continue,
    input wire show_mode,
    input wire punctually_report_en,
    input wire alarm_switch,
    input wire set_alarm_en,
    input wire set_alarm_time_hour,
    input wire set_alarm_time_minute,
    output reg [7:0] tubePosSignal,
    output reg [6:0] tubeShowSignal,
    output reg punctuallyReportSignal,
    output reg alarmReportSignal
);

    wire CLK_1k, CLK_1Hz, CLK_2Hz;
    wire secondInputSignal, minuteInputSignal, hourInputSignal;
    wire isPunctuallyReporting;
    wire [7:0] second, minute, hour;
    wire [6:0] secondOnesShowCode, secondTensShowCode,
    minuteOnesShowCode, minuteTensShowCode, hourOnesShowCode,
    hourTensShowCode;
    wire [6:0] alarmHourOnesShowCode, alarmHourTensShowCode,
    alarmMinuteOnesShowCode, alarmMinuteTensShowCode;
    wire secondToMinuteCarryBit, minuteToHourCarryBit;
    wire [4:0] hour_real_num;
    
```



```
reg [7:0] alarm_hour, alarm_minute;

FrequencyDivider_1k divider_1k(CP, CLK_1k);
FrequencyDivider_1hz divider_1Hz(CLK_1k, CR, clock_en,
CLK_1Hz);
FrequencyDivider_2hz divider_2Hz(CLK_1k, CR, clock_en,
CLK_2Hz);

TwoToOneSelector minuteInput(secondToMinuteCarryBit, CLK_1Hz,
~adjust_minute_en, minuteInputSignal);
TwoToOneSelector hourInput(minuteToHourCarryBit, CLK_1Hz,
~adjust_hour_en, hourInputSignal);
TwoToOneSelector secondInput(CLK_1Hz, 1'b0, ~adjust_hour_en
&& ~adjust_minute_en, secondInputSignal);

Counter_60 secondCounter(secondInputSignal, second_continue,
CR, second, secondToMinuteCarryBit);
Counter_60 minuteCounter(minuteInputSignal, clock_en, CR,
minute, minuteToHourCarryBit);
Counter_24 hourCounter(hourInputSignal, CR, clock_en,
hour[3:0], hour[7:4]);

assign hour_real_num = hour[3:0] + 10 * hour[7:4];
always @(*) begin
    alarm_hour = alarm_hour_set;
    alarm_minute = alarm_minute_set;
end

PunctuallyReporter PunctuallyReporter (minute, hour_real_num,
punctually_report_en, CLK_1Hz, isPunctuallyReporting,
punctuallyReportSignal);

TubeDecoder secondOnesDecoder(second[3:0],
secondOnesShowCode);
TubeDecoder secondTensDecoder(second[7:4],
secondTensShowCode);
TubeDecoder minuteOnesDecoder(minute[3:0],
minuteOnesShowCode);
TubeDecoder minuteTensDecoder(minute[7:4],
minuteTensShowCode);
TubeDecoder HourOnesDecoder(hour[3:0], hourOnesShowCode);
TubeDecoder hourTensDecoder(hour[7:4], hourTensShowCode);
TubeDecoder alarmMinuteOnesDecoder(alarm_minute[3:0],
alarmMinuteOnesShowCode);
```

```

        TubeDecoder alarmMinuteTensDecoder(alarm_minute[7:4],
alarmMinuteTensShowCode);
        TubeDecoder alarmHourOnesDecoder(alarm_hour[3:0],
alarmHourOnesShowCode);
        TubeDecoder alarmHourTensDecoder(alarm_hour[7:4],
alarmHourTensShowCode);

        TubeShower shower(CLK_1k, CLK_2Hz, show_mode, ~set_alarm_en,
isPunctuallyReporting, hour_real_num, hour,
                        secondOnesShowCode, secondTensShowCode,
minuteOnesShowCode, minuteTensShowCode,
                        hourOnesShowCode, hourTensShowCode,
alarmHourTensShowCode, alarmHourOnesShowCode,
                        alarmMinuteTensShowCode,
alarmMinuteOnesShowCode, tubePosSignal, tubeShowSignal);

        AlarmReporter alarmReporter(alarm_switch, alarm_hour,
alarm_minute, hour, minute, CLK_1Hz, alarmReportSignal);
        AlarmSetter alarmSetter(set_alarm_time_hour && ~set_alarm_en,
set_alarm_time_minute && ~set_alarm_en, CLK_1Hz, alarm_hour_set,
alarm_minute_set);

    endmodule

```

2. 分频为 1khz

```

`timescale 1ns / 1ps

module FrequencyDivider_1k(
    input CP,
    output reg CLK_1k = 0
);
    reg [15:0] state;
    always @(posedge CP)
        begin
            // for real use
            if (state < 49999) state <= state + 1'b1;
            // for sim
            // if (state < 4) state <= state +1'b1;
            else
                begin
                    state <= 0;
                    CLK_1k <= ~CLK_1k;
                end
        end
end

```

```
endmodule
```

3. 分频为 1hz

```
`timescale 1ns / 1ps
```

```
module FrequencyDivider_1hz(
    input CLK_1k,
    input CR,
    input EN,
    output reg CLK_1Hz = 0
);
    reg [8:0] state;
    always @(posedge CLK_1k or negedge CR)
        begin
            if (~CR)
                begin
                    CLK_1Hz <= 0;
                    state <= 0;
                end
            else if (~EN)
                begin
                    CLK_1Hz <= CLK_1Hz;
                    state <= state;
                end
            // for real use, here should be 499, but for test, we can
            // change it into 49 or 4
            else if (state < 499) state <= state + 1'b1;
            // else if (state < 49) state <= state + 1'b1;
            // else if (state < 4) state <= state + 1'b1;
            else
                begin
                    state <= 0;
                    CLK_1Hz <= ~CLK_1Hz;
                end
        end
    end
endmodule
```

4. 二选一选择器

```
module TwoToOneSelector(
    input inputA,
    input inputB,
    input selectSignal,
```

```

        output reg outputSignal
    );
    always @(*)
        begin
            if(selectSignal == 1'b0)
                outputSignal <= inputA;
            else
                outputSignal <= inputB;
        end
    endmodule

```

5.60 计数器

```
`timescale 1ns / 1ps
```

```

module Counter_60(
    input CP,
    input EN,
    input CR,
    output reg [7:0] Q,
    output reg carryBit
);
    wire onesToTensCarryBit;
    wire tensToUpperCarryBit;
    wire [3:0] ones, tens;
    Counter_10 OnesPlace(CP, CR, EN, ones, onesToTensCarryBit);
    Counter_6
    TensPlace(onesToTensCarryBit, CR, EN, tens, tensToUpperCarryBit);
    always @(*) Q = {tens[3:0], ones[3:0]};
    always @(*) carryBit = tensToUpperCarryBit;
endmodule

```

6.24 计数器

```

`timescale 1ns / 1ps
module Counter_24(CP, CR, EN, Q_ones, Q_tens);
    input CP;
    input CR;
    input EN;
    output reg [3:0] Q_ones = 4'b0000;
    output reg [3:0] Q_tens = 4'b0000;

    always @(posedge CP or negedge CR)
        begin

```

```

        if (~CR)
            begin
                Q_ones <= 4'b0000;
                Q_tens <= 4'b0000;
            end
        else if (~EN)
            begin
                Q_ones <= Q_ones;
                Q_tens <= Q_tens;
            end
        else if (Q_ones == 4'b1001 && Q_tens < 4'b0010)
            begin
                Q_ones <= 4'b0000;
                Q_tens <= Q_tens + 1'b1;
            end
        else if (Q_ones == 4'b0011 && Q_tens == 4'b0010)
            begin
                Q_tens <= 4'b0000;
                Q_ones <= 4'b0000;
            end
        else
            begin
                Q_ones <= Q_ones + 1'b1;
            end
        end
    end
endmodule

```

6. 整点&&闹钟显示

```

`timescale 1ns / 1ps

module PunctuallyReporter(
    input [7:0] minute,
    input [4:0] hour,
    input EN,
    input CLK_1Hz,
    output reg isReporting = 0,
    output reg reportSignal = 0
);
    reg [5:0] flashingTime = 0;
    reg hasReport = 0;
    always @(posedge CLK_1Hz)
        begin
            if (EN == 0) reportSignal = 1'b0;
            else if (minute[7:0] == 0 && flashingTime < 2 *

```

```

(hour[4:0]) && hasReport == 1'b0)
    begin
        reportSignal <= ~reportSignal;
        flashingTime <= flashingTime + 1'b1;
    end
else
    begin
        reportSignal <= 1'b0;
        flashingTime <= 1'b0;
        hasReport <= 1'b1;
    end

    if (minute[7:0] > 0)
        hasReport <= 1'b0;
    if (flashingTime > 0)
        isReporting <= 1;
    else isReporting <= 0;
end
endmodule

```

7. 译码显示

```

`timescale 1ns / 1ps

module TubeDecoder (
    input [3:0] number,
    output reg [6:0] code
);
    always @(number)
        begin
            case(number)
                4'd0: code <= 7'b100_0000;
                4'd1: code <= 7'b111_1001;
                4'd2: code <= 7'b010_0100;
                4'd3: code <= 7'b011_0000;
                4'd4: code <= 7'b001_1001;
                4'd5: code <= 7'b001_0010;
                4'd6: code <= 7'b000_0010;
                4'd7: code <= 7'b111_1000;
                4'd8: code <= 7'b000_0000;
                4'd9: code <= 7'b001_0000;

                4'ha: code <= 7'b000_1000;//show A
                4'hb: code <= 7'b000_1100;//show P
                default: code <= 7'b111_1111;
            endcase
        end
endmodule

```

```

        endcase
    end
endmodule

```

8. 亮灯逻辑

```

`timescale 1ns / 1ps

module TubeShower(
    input CLK_1k,
    input CLK_2Hz,
    input showMode,//for show mode 0, 24h mode clock;mode 1, 12h
mode clock
    input isSettingAlarm,
    input isPunctuallyReporting,// when is punctually reporting
HH:mm flashes per 0.5 Sec,last two bit show flash time
    input [4:0] hour_real_num,//lower 4 bits are for hour ones
bit,upper 4 bits are for hour tens bit
    input [7:0] hour,
    input [6:0] second_ones,
    input [6:0] second_tens,
    input [6:0] minute_ones,
    input [6:0] minute_tens,
    input [6:0] hour_ones,
    input [6:0] hour_tens,
    input [6:0] alarm_hour_setting_tens,
    input [6:0] alarm_hour_setting_ones,
    input [6:0] alarm_minute_setting_tens,
    input [6:0] alarm_minute_setting_ones,
    output reg [7:0] tubePos,
    output reg [6:0] showCode
);
    integer k = 0;
    wire [6:0] convert0;
    wire [7:0] hour_12;
    reg [3:0] convert_ones,convert_tens;
    always@ (*)
    begin
        if (hour_real_num == 5'd20 || hour_real_num == 5'd21)
            convert_ones <= hour[3:0] + 8;
        else
            convert_ones <= hour[3:0] - 2;
    end
end

```

```

TubeDecoder decoder0(convert_ones, convert0);

always @(posedge CLK_1k)
    begin
        case(k)
            0:
                // show A or P or none for 12/24 hour switch or
                noting when set alarm
                begin
                    tubePos <= 8'b1111_1110;
                    // when is setting alarm, show nothing
                    if (isSettingAlarm) showCode <=
7'b111_1111;
                    // when is punctually reporting, show hour
                    ones bit
                    else if (isPunctuallyReporting) showCode
<= hour_ones;
                    else if (showMode == 0) showCode <=
7'b111_1111;
                    else if (showMode == 1)
                        begin
                            if (hour_real_num >= 5'd12)
showCode <= 7'b000_1100;
                                else showCode <= 7'b000_1000;
                            end
                            k <= k + 1;
                        end
                1:
                    // show nothing
                    begin
                        tubePos <= 8'b1111_1101;
                        // when is punctually reporting, show hour
                        tens bit
                        if (isPunctuallyReporting) showCode <=
hour_tens;
                        else showCode <= 7'b111_1111;
                        k <= k + 1;
                    end
                2:
                    // show second ones bit or noting when set alarm
                    begin
                        tubePos <= 8'b1111_1011;
                        if (isSettingAlarm) showCode <=
7'b111_1111;
                    end
        endcase
    end

```



```

        else
            begin
                showCode <= second_ones;
            end
            k <= k + 1;
        end
3:
//      show second tens bit or noting when set alarm
        begin
            tubePos <= 8'b1111_0111;
            if (isSettingAlarm) showCode <=
7'b111_1111;

            else
                begin
                    showCode <= second_tens;
                end
                k <= k + 1;
            end
4:
//      show minute ones bit
        begin
            tubePos <= 8'b1110_1111;
            if (isSettingAlarm) showCode <=
alarm_minute_setting_ones;

            else if (isPunctuallyReporting)
                begin
                    if (CLK_2Hz == 1'b1) showCode <=
minute_ones;

                    else showCode <= 7'b111_1111;
                end
            else showCode <= minute_ones;
            k <= k + 1;
        end
5:
//      show mintue tens bit
        begin
            tubePos <= 8'b1101_1111;
            if (isSettingAlarm) showCode <=
alarm_minute_setting_tens;

            else if (isPunctuallyReporting)
                begin
                    if (CLK_2Hz == 1'b1) showCode <=
minute_tens;

                    else showCode <= 7'b111_1111;

```

```

        end
        else showCode <= minute_tens;
        k <= k + 1;
    end
6:
    // show hour ones bit
    begin
        tubePos <= 8'b1011_1111;
        if (isSettingAlarm) showCode <=
alarm_hour_setting_ones;
        else if (isPunctuallyReporting)
            begin
                if (CLK_2Hz == 1'b0) showCode <=
7'b111_1111;
                else
                    begin
                        if (showMode == 0 ||
hour_real_num <= 5'd12)
                            showCode <=
hour_ones;
                        else if (showMode == 1 &&
hour_real_num > 5'd12)
                            showCode <= convert0;
                    end
                end
            end
        else
            begin
                if (showMode == 0 ||
hour_real_num <= 5'd12)
                    showCode <= hour_ones;
                else if (showMode == 1 &&
hour_real_num > 5'd12)
                    showCode <= convert0;
                end
            end
        k <= k + 1;
    end
7:
    // show hour tens bit
    begin
        tubePos <= 8'b0111_1111;
        if (isSettingAlarm) showCode <=
alarm_hour_setting_tens;
        else if (isPunctuallyReporting)
            begin

```

```

        if (CLK_2Hz == 1'b0) showCode <=
7'b111_1111;
        else
            if (showMode == 0 ||
hour_real_num <= 5'd12) showCode <= hour_tens;
            else if (showMode == 1)
                begin
                    if (hour_real_num <
5'd22 && hour_real_num > 5'd12)
                        showCode <=
7'b100_0000;
                    else
                        showCode <=
7'b111_1001;
                end
            end
        else
            begin
                if (showMode == 0 ||
hour_real_num <= 5'd12) showCode <= hour_tens;
                else if (showMode == 1)
                    begin
                        if (hour_real_num < 5'd22
&& hour_real_num > 5'd12)
                            showCode <=
7'b100_0000;
                        else
                            showCode <=
7'b111_1001;
                    end
                end
            end
        k <= k + 1;
    end
8: k <= 0;
endcase
end
endmodule

```

9. 闹钟响铃

```
`timescale 1ns / 1ps
```

```
module AlarmReporter(
```

```

    input EN,
    input [7:0] hour_set_num,
    input [7:0] minute_set_num,
    input [7:0] hour_current_num,
    input [7:0] minute_current,
    input CLK_1Hz,
    output reg reportSignal = 0
);
always @(posedge CLK_1Hz)
    begin
        if (EN == 0)
            reportSignal <= 1'b0;
        else if (hour_current_num == hour_set_num &&
minute_current == minute_set_num)
            reportSignal <= ~reportSignal;
        else
            reportSignal <= 1'b0;
    end
endmodule

```

10. 闹钟设置

```
`timescale 1ns / 1ps
```

```

module AlarmSetter(
    input set_hour_en,
    input set_minute_en,
    input CLK_1Hz,
    output reg [7:0] hour_set = 8'b0000_0000,
    output reg [7:0] minute_set = 8'b0000_0000
);
    reg onesToTensCarryBit;
    always @(posedge CLK_1Hz) begin
        if (~set_minute_en) minute_set[3:0] <= minute_set[3:0];
        else if (minute_set[3:0] == 4'b1001)
            begin
                minute_set[3:0] <= 4'b0000;
                onesToTensCarryBit = 1'b1;
            end
        else
            begin
                minute_set[3:0] <= minute_set[3:0] + 1'b1;
                onesToTensCarryBit = 1'b0;
            end
    end
endmodule

```

```
        end
    end

    always @(posedge onesToTensCarryBit) begin
        if (~set_minute_en) minute_set[7:4] <= minute_set[7:4];
        else if (minute_set[7:4] == 4'b0101)
            minute_set[7:4] <= 4'b0000;
        else
            minute_set[7:4] <= minute_set[7:4] + 1'b1;
        end

    always @(posedge CLK_1Hz) begin
        if (~set_hour_en) hour_set <= hour_set;
        else if (hour_set[3:0] == 4'b1001 && hour_set[7:4] <
4'b0010)
            begin
                hour_set[3:0] <= 4'b0000;
                hour_set[7:4] <= hour_set[7:4]+1'b1;
            end
        else if (hour_set[3:0] == 4'b0011 && hour_set[7:4] ==
4'b0010)
            hour_set = 8'b0000_0000;
        else
            hour_set[3:0] <= hour_set[3:0] + 1'b1;
        end
    end
endmodule
```

六、实验小结

通过这次实验，我深刻体验到了数字电路设计的难度。在实验过程中，我不断尝试、纠错，逐渐掌握了 Vivado 等软件的使用方法，并领悟了数字电路软件设计的方法论。这次实验让我对常见错误和设计重点有了更深入的理解，为我后续课程的学习打下了坚实的基础。虽然数字钟实验十分考验细致和全面考虑的能力，但我相信通过这样的实践，后面的学习会更加顺利。